

HOMEWORK 2.**Due: Friday, March 8, 2019.****This is an individual assignment!****1. Extracting and simulating the synthesized design.**


In the first lab, we have created a design by using a strictly digital ('VLSI') design flow. In this assignment, we will inspect the results of the static timing analysis.

To do this, please work through Lab 2, then turn in:

- For the path A[2] rise to Z[15] rise, report the delay measured by IC Compiler.
- A screenshot of the critical path highlighted in IC Compiler showing the wires that contribute to the path from a).
- For the functional testbench that counts from A=0000 to A=1111, report the power measured by Primetime.
- A screenshot of your decoder layout imported into Virtuoso after running it through the HAMMER flow.

 
2. Delays

Consider an inverter driving a capacitive load in 28nm bulk-CMOS technology.



All transistors are minimum length and $W_n = 0.5\mu\text{m}$, $W_p = 1\mu\text{m}$, $V_{DD} = 1\text{V}$. In this technology, $C_g = C_d = 2\text{fF}/\mu\text{m}$, transistor thresholds are 0.25V and fanout-of-4 inverter delay is 15ps.

 - For what range of sizes of the load capacitor, C_L , adding another inverter to drive the load reduces the delay?
- If the input capacitance of the first inverter in figure below is set to $C_1 = 3\text{fF}$, the wire capacitance C_w is 6fF, how would you size the second inverter that is driving 13.5fF load to minimize the overall delay from *In* to *Out*? Is this result intuitive?



3. Switching trajectories

In the I_{DS} - V_{DS} coordinates, plot simulated switching trajectories for the following transistors:

- a) NMOS transistor in an inverter chain with a fanout of 1.
- b) NMOS transistor in an inverter chain with a fanout of 4.
- c) Top NMOS transistor in the 2-input NAND gate with a fanout of 3.
- d) Bottom NMOS transistor in the 2-input NAND gate with a fanout of 3.